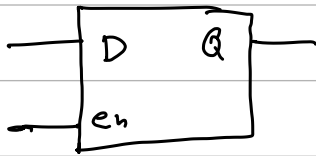


Reading 9

LATCH Video


• Basic Latch!



• if en is 1, then Q is whatever D is.


• if en is 0, then Q is whatever D was when en was flipped to 0.

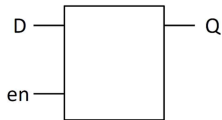↳ Now even if you change D, Q does not change.




en	D	Q
0	0	hold
0	1	hold
1	0	0
1	1	1

• SR Latch

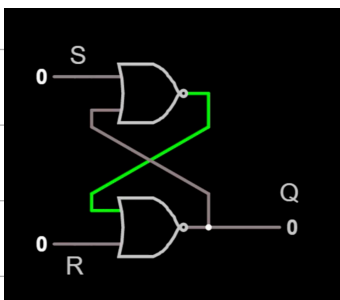

• S is the set control input

• R is the reset control input

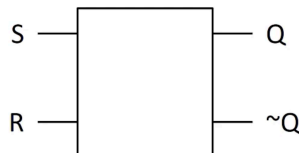


S	R	Q	~Q
0	0	hold	hold
0	1	1	0
1	0	0	1
1	1	0	0

← mostly want to avoid this situation

D-Latch

- Appending some D logic to an SR latch.

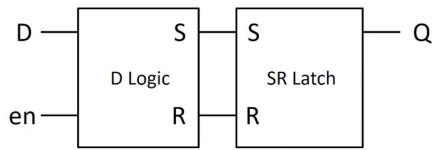

en	D	Q	S	R
0	0	hold	0	0
0	1	hold	0	0
1	0	0	0	1
1	1	1	1	0

$$S = en D$$

$$R = en D'$$

• Note: A circuit with an odd number of inverters in a loop will oscillate

• Note: An even number of inverters in a loop will take on a stable value of 1 or 0.

FIIP FLOP Video

- Latches are problematic
 - ↳ Since they cause continuous oscillation when 'enable = 1' in some circuits.
- Flip Flops help resolve this issue.
 - ↳ They have clocks instead of enables.
- Analogy: you want to carry in groceries, but dog wants to go out.
 - ↳ If you only have one door it's a latch (the dog always gets out)
 - ↳ If you have 2 doors (i.e. utility room), you can get groceries in without letting dog out. This is the behavior of a flip flop.


• You can build a flip-flop from from a pair of latches:

↳ First latch enabled when clock is low (flip)


↳ Second latch enabled when clock is high (flop)

• Diagram (Sequence):

1.

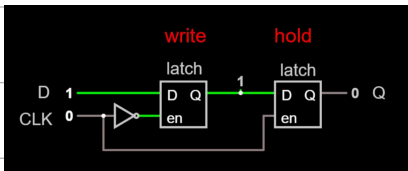


2.

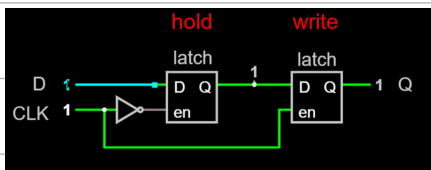

→ here even if $D=0$, the midpoint = $Q=1$

3.

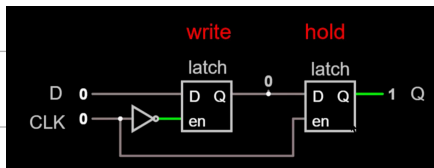

• Note: An individual latch in a flip-flop can go transparent but the entire flip flop will never go transparent.